

Professor Oldham

Fall 1999

**EECS 40 — MIDTERM #1**

29 September 1999

Name: \_\_\_\_\_  
Last, First

Student ID: \_\_\_\_\_

TA:  Kusuma  
 Chang

**Guidelines:**




1. Closed book and notes except 1 page of formulas.
2. You may use a calculator.
3. Do not unstaple the exam.
4. Show *all your work and reasoning on the exam* in order to receive full or partial credit.
5. This exam contains 12 pages plus the cover page and 2 sheets of scratch paper included at the end of the exam. You can remove these from the rest of the exam if you wish.

Problem	Points Possible	Your Score
1	20	
2	15	
3	15	
4	20	
5	15	
6	15	
<b>Total</b>	<b>100</b>	

$K = 10^3$
$m = 10^{-3}$
$\mu = 10^{-6}$
$n = 10^{-9}$
$p = 10^{-12}$
$f = 10^{-15}$

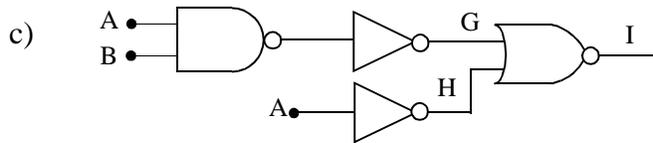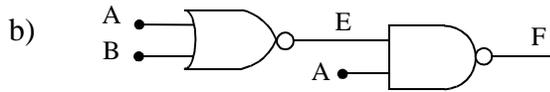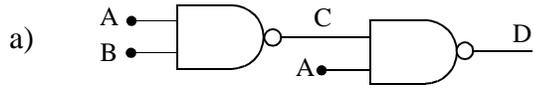**Problem 1 “Static Logic” (20 points)**

Fill in the logic values in the table below for input values given. Note that the value for “C” is given as an example.







Fill in boxes →  
(zero or 1)

	Intermediate Values and Outputs for A = 1, B = 0						
	C	D	E	F	G	H	I
Value	1						

**Prob. 1 (cont.)**

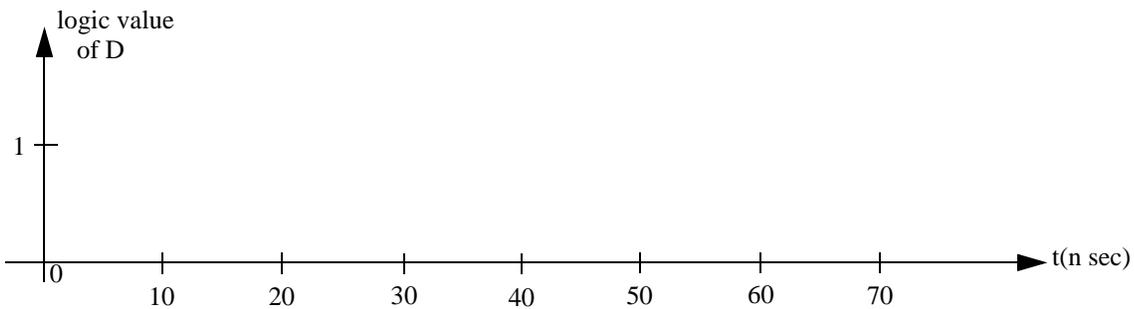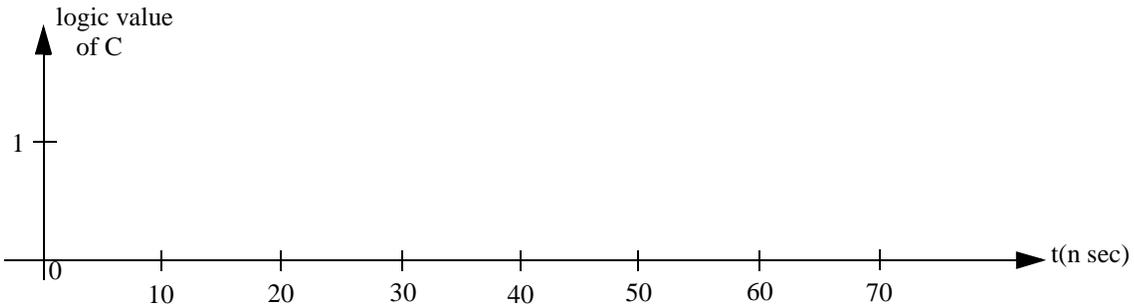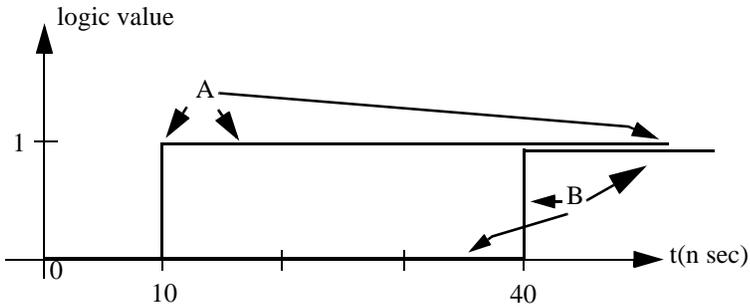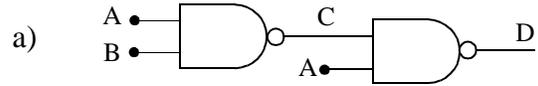
e) All logic blocks in the above figures have a unit gate delay of 10n sec.

Show the logic values versus time (for  $t = 0$  to 70n sec) for outputs C and D of example a), given the logic input values (A and B) shown below:




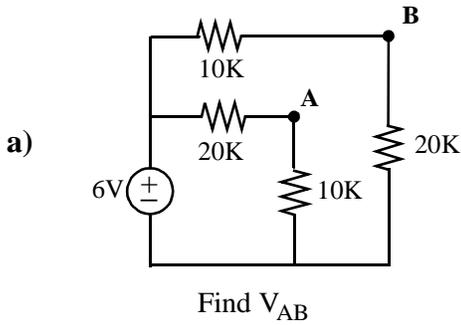**Problem 2 “Circuit Solution by Inspection” (15 points)**


Each of these problems should take no more than 1-2 minutes. WRITE ANSWER IN PLACE PROVIDED. There is no partial credit on these mini-problems.



$$V_{AB} = \text{_____ V}$$

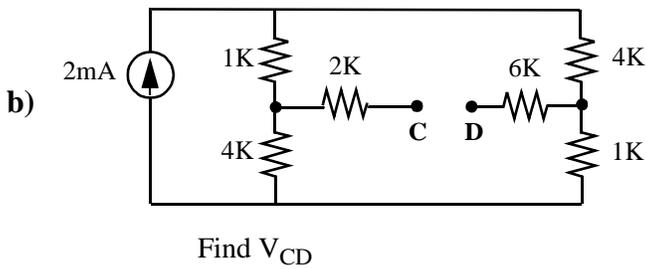


$$V_{CD} = \text{_____ V}$$

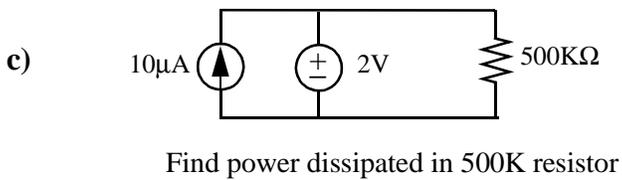


$$P = \text{_____ W}$$


**Problem 2 (cont.)**

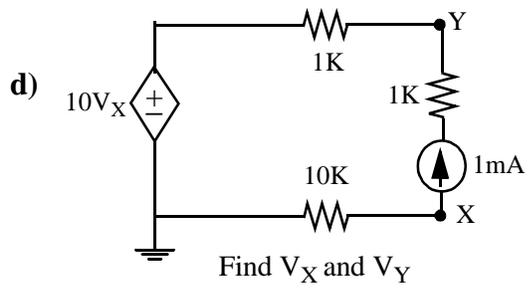

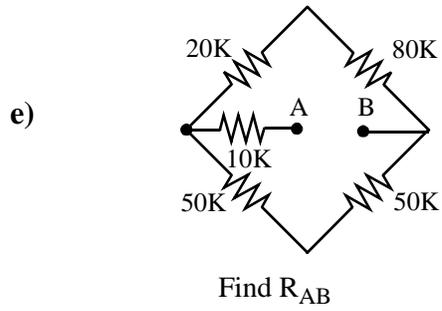
$V_X = \underline{\hspace{2cm}} \text{ V}$
$V_Y = \underline{\hspace{2cm}} \text{ V}$



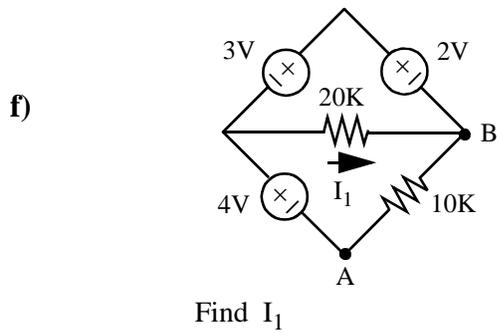$R_{AB} = \underline{\hspace{2cm}} \text{ K}\Omega$
---



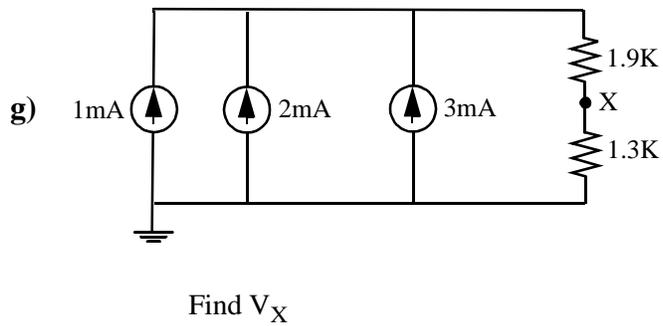
$I_1 = \underline{\hspace{2cm}} \mu\text{A}$
--




$V_X = \underline{\hspace{2cm}} \text{ V}$
--

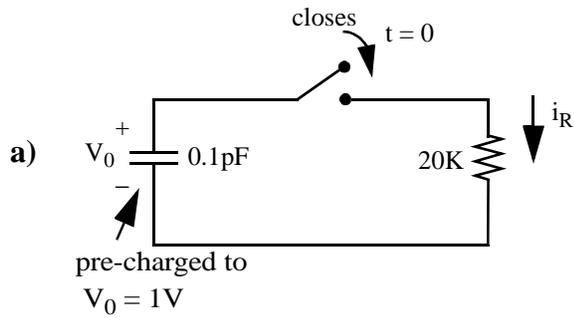**Problem 3 “Initial Conditions” (15 points)**


In each of the problems below, find the value of the current or voltage just after the switch moves ( $t = 0^+$ ). (What is requested is just a numerical value, NOT an equation or function of time.)




$$i_R = \text{_____ } \mu A$$

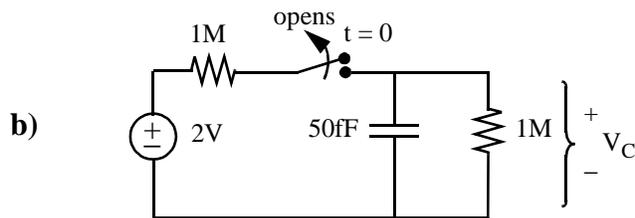

$$V_C = \text{_____ } V$$

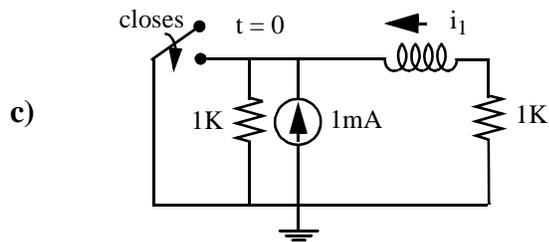

$$i_1 = \text{_____ } mA$$

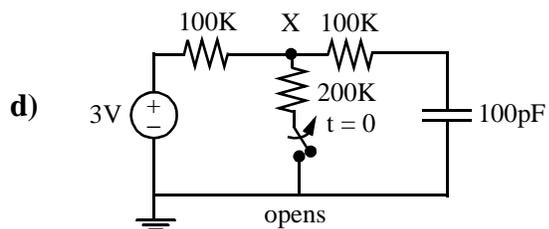


$$V_X = \text{_____ } V$$

Problem 3 Worksheet

**Problem 4 “Nodal Analysis” (20 points)**

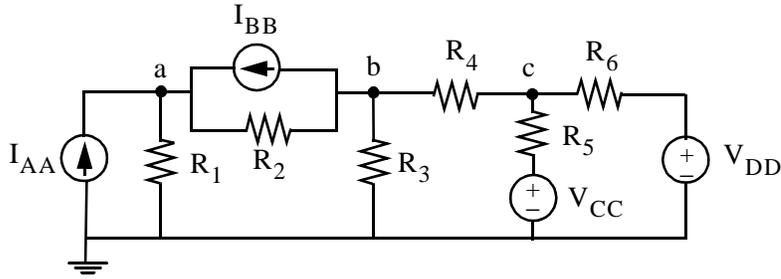- a. For the circuit below you are asked to write sufficient equations to find the unknowns. **You MUST put the equations into the space indicated.** Do any scratch work on the page opposite. **Do not solve.**




Unknowns:  $V_a, V_b, V_c$

Write final equations here:

<hr/> <hr/> <hr/>
-------------------

**Problem 4 (cont.)**

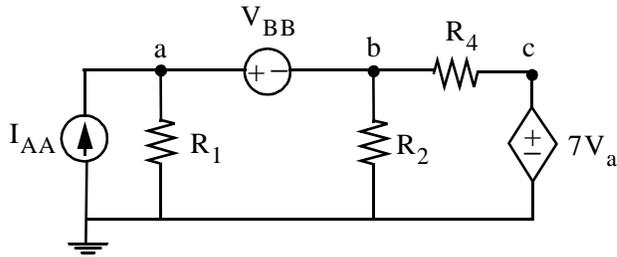- b. Similar to part a, you are asked to write sufficient equations to find the unknowns. Do not solve. **You must** put the equations in the space indicated below.




Unknowns:  $V_a, V_b, V_c$

Put final form for equations here:

<hr/> <hr/> <hr/>
-------------------

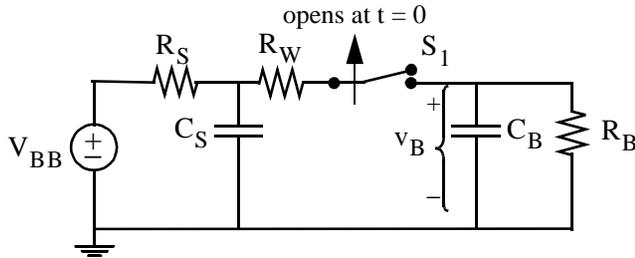**Problem 5** (15 points)

The following circuit is used to study one phase of the operation of a DRAM cell — the slow decay of a stored “1”. First the switch  $S_1$  is closed and kept closed to write a “1”. Then it opens and the storage capacitor  $C_B$  is supposed to maintain the stored information. In this memory, a valid “1” is any voltage  $v_B$  in the range of 1 to 3V.



- $V_{BB} = 2V$
- $C_S = 100\text{pf}$
- $C_B = 50\text{fF}$
- $R_S = 10K$
- $R_B = 10^{13}\Omega$
- $R_W = 100\Omega$

a) What is the value of  $v_B$ , just after the switch  $S_1$  opens, i.e., at  $t = 0^+$ ? (1% accuracy is sufficient.)

$v_B = \text{_____} V$


b) What is the value of  $v_B$  much later (e.g., 1 hour later)?

$v_B = \text{_____} V$

c) On the axes provided on the facing page, neatly sketch the graph of  $v_B(t)$  versus time. **You must label axes with units.**



d) Write an equation for  $v_B$  as a function of time.

Problem 5 (cont.)

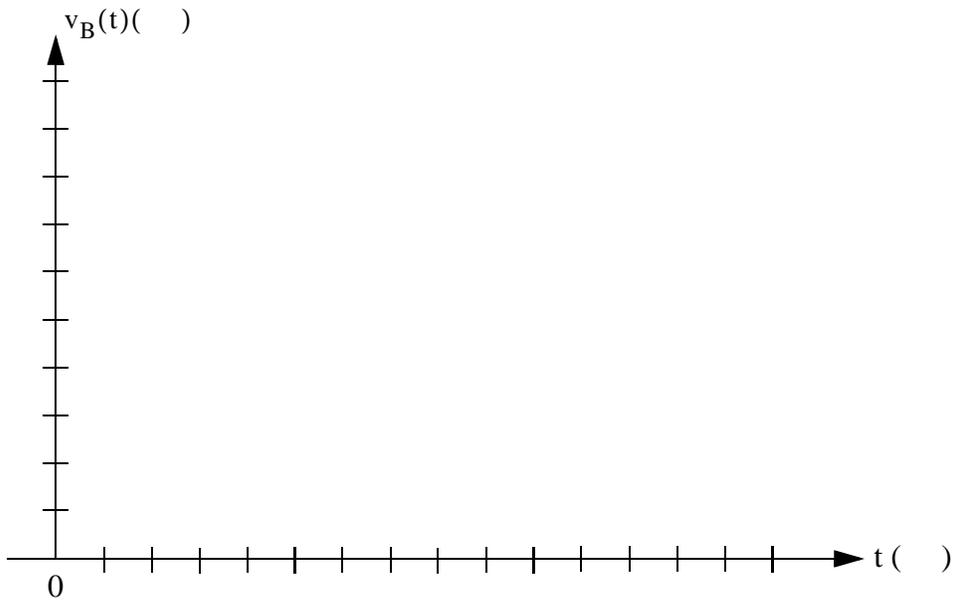

**Problem 6** (15 points)

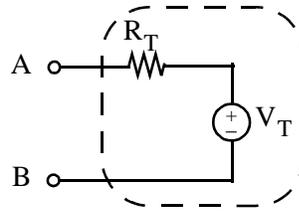
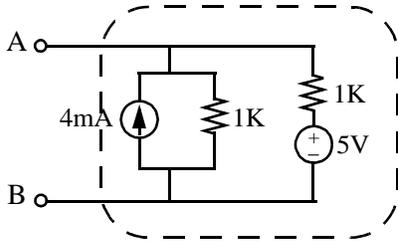
a) Find the Thévenin Equivalent Circuit of the following:



$$V_T = \text{_____ V}$$

$$R_T = \text{_____ K}$$

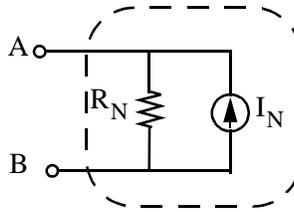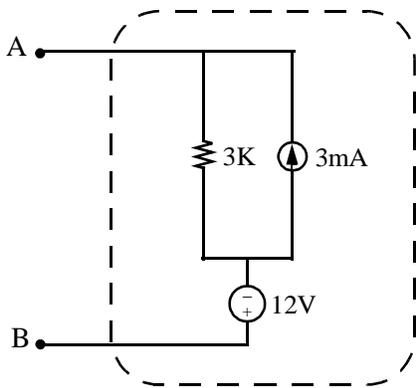
b) Find the Norton Equivalent of the following linear circuit:



$$I_N = \text{_____ mA}$$

$$R_N = \text{_____ K}$$

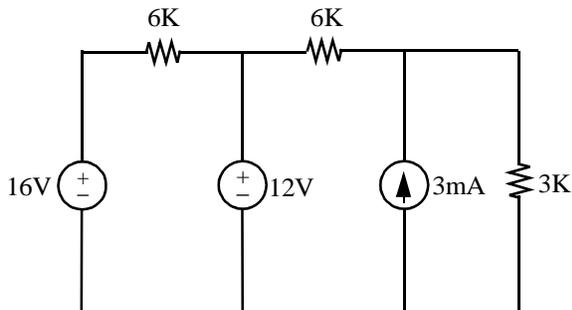c) Find the power supplied by the 12V voltage source in the following circuit.



$$\text{Power out} = \text{_____ W}$$

Problem 6 Worksheet