

Professor Oldham

Spring 2001

EECS 42 — MIDTERM #1

22 February 2001

Name: Einstein A
Last, First

Student ID: _____

Signature: _____

SOLUTIONS

Guidelines:

1. Closed book. A 2-page summary sheet with formulas is provided at the end of the exam.
2. Show *all your work and reasoning on the exam* in order to receive credit.
3. **Warning:** Some problems will be graded with no partial credit, so check your answers.
4. You may use a calculator.
5. Do not unstaple the exam.
6. This exam contains 5 problems worth 20 points each, and corresponding worksheets plus the cover page and the 2-page summary sheet.
7. **Please do not ask questions** except to point out possible errors or typographical mistakes.

Problem	Points Possible	Your Score
1	20	
2	20	
3	20	
4	20	
5	20	
Total	100	

Problem 1 (20 points)

In the circuit below we are interested in the voltage at nodes X and Y and use nodal analysis.

(a) Some possible nodal equations are given below. Circle the equation that is correct. (If none are correct, then correct one and circle it.)

(a.1) $V_1/R_1 - I_1 - V_X/R_2 = I_2 - V_Y/R_3$


(a.2) $V_1/R_1 + V_3/R_4 = 0$

(a.3) $I_1 + I_2 + V_1/R_1 + V_3/R_4 + V_3/R_3 = 0$

(a.4) $V_1/R_1 + I_1 - V_X/R_2 + I_2 + (V_3 - V_Y)/R_4 = 0$

(a.5) $(V_1 - V_X)/R_1 + I_1 - V_X/R_2 = -I_2 + (V_Y - V_3)/R_4$

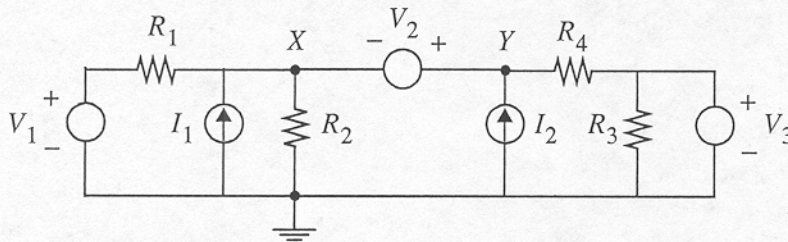(a.6) $(V_1 - V_X)/R_1 + I_1 - V_X/R_2 = (V_2 - V_3)/R_4$



(b) What other equation, if any, is needed to solve for V_X and V_Y ? Write it in the box below, BUT DO NOT SOLVE for V_X and V_Y .


Answer here →

$$V_X + V_2 = V_Y$$

Problem 1 Worksheet

floating voltage source

a)

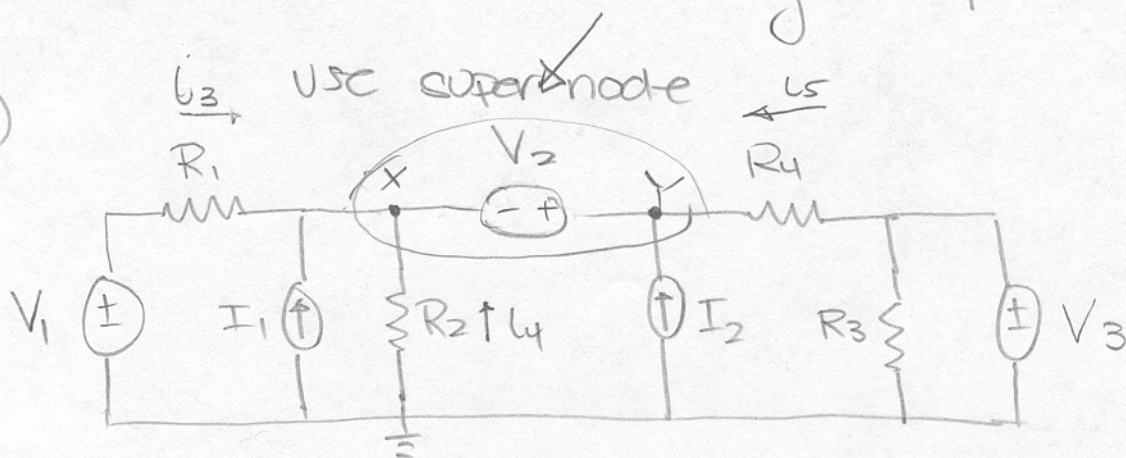

Super node equation (sum currents in = 0)

$$I_1 + I_2 + I_3 + I_4 + I_5 = 0$$

$$\Rightarrow I_1 + I_2 + \frac{V_1 - V_x}{R_1} + \frac{0 - V_x}{R_2} + \frac{V_3 - V_y}{R_4} = 0$$

by process of elimination, only

$$\text{a.s.} : \frac{V_1 - V_x}{R_1} + I_1 - \frac{V_x}{R_2} = -I_2 + \frac{V_3 - V_y}{R_4}$$

$I_3 \quad I_1 \quad I_4 \quad -I_2 \quad -I_5$

matches with nodal equation.

b) Auxiliary equation


find relationship between V_x and V_y

|| V_x goes up V_2 to get to V_y

$$\therefore V_x + V_2 = V_y$$

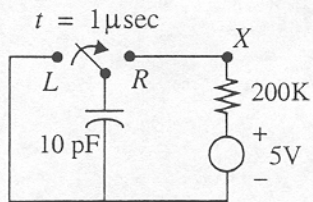Problem 2 (20 points)

In the circuit below, the switch is operated at $t = 1\mu\text{sec}$ (in other words, the capacitor is switched from node L to node R).



(a) Find V_X , the voltage at node X , for $t < 1\mu\text{sec}$.

(Note: Answer must be in the box.)

a) $V_X = 5\text{ V}$

(b) Find V_X for $t = 1\mu\text{sec}$ (just after switch moves).

(Note: Answer must be in the box.)

b) $V_X = 0\text{ V}$


(c) Find V_X for $t \rightarrow \infty$.

(Note: Answer must be in the box.)

c) $V_X = 5\text{ V}$

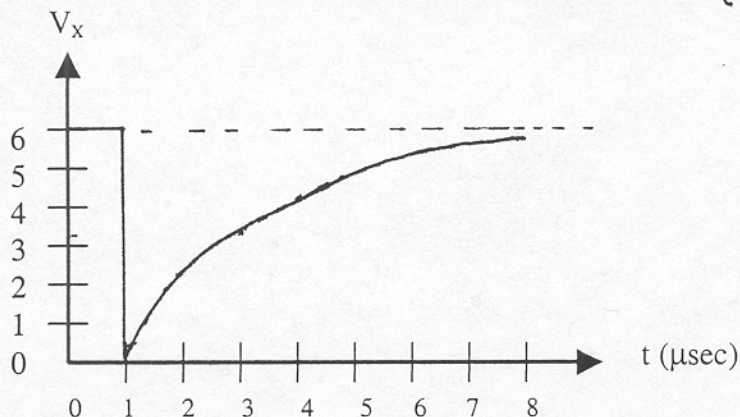(d) Sketch neatly on the axes below a plot of V_X versus time.

(Warning: Neatness and accuracy will be rewarded.)




$$\tau = RC = 2\mu\text{s}$$

Problem 2 Worksheet

(a). When switch is on the left
Circuit is shown on the right:

$V_x = 5V$. since no current goes through the resistor, $V_{xy} = 0$.

$$V_x = 5V.$$

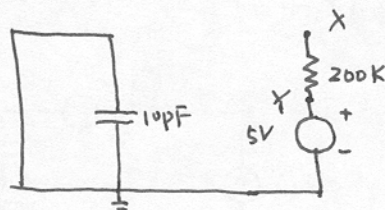


(b). The voltage across the capacitor is now 0.

Just after the switch is turned to the right.

Notice now V_x is the voltage across the capacitor. We know voltage across capacitor can't jump.

$$V_x = 0$$

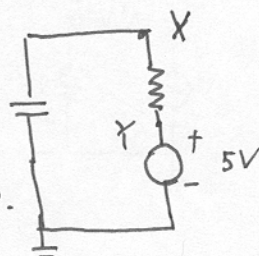


(c). For $t \rightarrow \infty$, no current goes through the loop.

So again $V_x = V_y = 5v$.

(d). Time Constant $\tau = 2 \mu s$.

$t < 1 \mu s$, $V_x = 5V$.

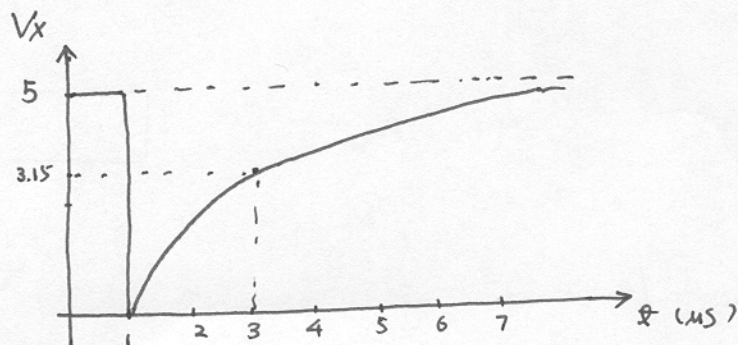
$1 < t < \infty \mu s$, $V_x = 5(1 - e^{-(t-1)/\tau})$, $\tau = 2 \mu s$.



Problem 3 (20 points)

Find the voltage indicated for each of the following circuits. (The answer MUST be in the box provided.)

(a) Find V_A .

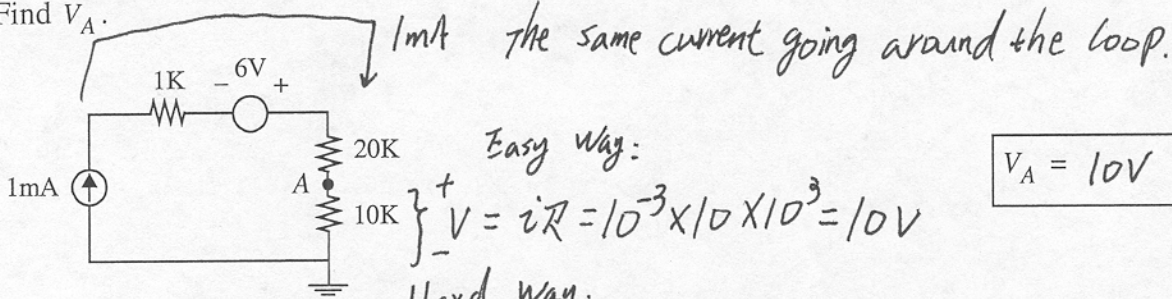


Easy way:


$$V = iR = 10^{-3} \times 10 \times 10^3 = 10V$$

$V_A = 10V$

Hard way:

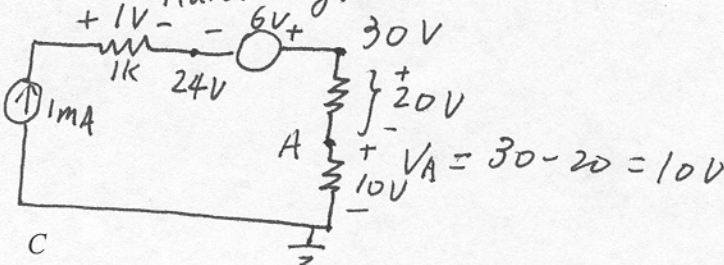

(b) Find V_{BC} .

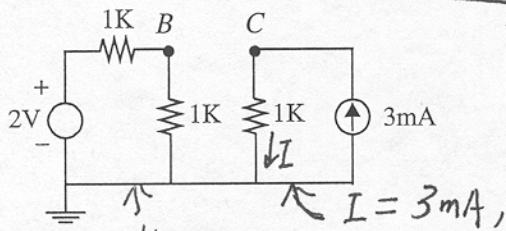

Voltage Divider:


$$V_B = \left(\frac{1}{1+1}\right) \cdot 2V = 1V$$

$$V_C = IR = 3mA \times 1K = 3V$$

$$V_{BC} = V_B - V_C = -2V$$

$V_{BC} = -2V$

(c) Find V_D . 2mA

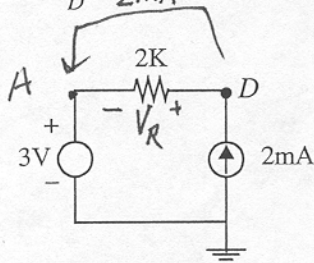

$$V_A = 3V,$$


$$V_R = IR = 2mA \times 2K = 4V$$

current flowing from high voltage to low voltage

$$V_D = V_A + V_R = 3 + 4 = 7V$$

$V_D = 7V$

(d) Find V_E .

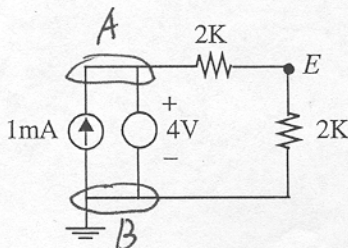

Voltage drop between A and B

is determined by the voltage source.

$$V_{AB} = 4V$$

current source does not change this.

$$\text{Voltage divider: } V_E = \left(\frac{2K}{2K+2K}\right) \cdot V_{AB} = \frac{1}{2} \cdot 4V = 2V$$

V_E is the voltage across the 2K resistor on the right

$V_E = 2V$

Problem 4 (20 points)

For the circuit below, calculate the following quantities. (Note that the sign is important and the answer must appear in the box.) This is a DC, not a transient, problem.

(a) P_1 , the power into (dissipated in) resistor R_1 . 3 methods

$P_1 = 3.6 \text{ mW}$

#1 $P = \frac{V^2}{R} = \frac{(6V)^2}{10K} = 3.6 \text{ mW}$

#3 $P = iV = (0.6 \text{ mA})(6V) = 3.6 \text{ mW}$

#2 $i = \frac{6V}{10K} = 0.6 \text{ mA}$
 $P = i^2 R = (0.6 \text{ mA})^2 (10K) = 3.6 \text{ mW}$

(b) P_2 , the power into (dissipated in) resistor R_2 . 3 methods

$P_2 = 10^{-7} \text{ W}$
 $= 0.1 \mu\text{W}$
 $= 100 \text{ nW}$

#1 $P = i^2 R = (1 \mu\text{A})^2 (100K) = 1 \times 10^{-7} \text{ W}$

#3 $P = \frac{V^2}{R} = \frac{(0.1V)^2}{100K} = 1 \times 10^{-7} \text{ W}$

$V_{R_2} = (1 \mu\text{A})(100K) = 0.1V$

#2 $P = IV = (1 \mu\text{A})(0.1V) = 1 \times 10^{-7} \text{ W}$

(c) P_3 , the power into capacitor C_3 .

$P_3 = 0 \text{ W}$


This is a DC, not a transient problem.
 Steady State! No current through capacitor

$P = IV = 0 \text{ W}$

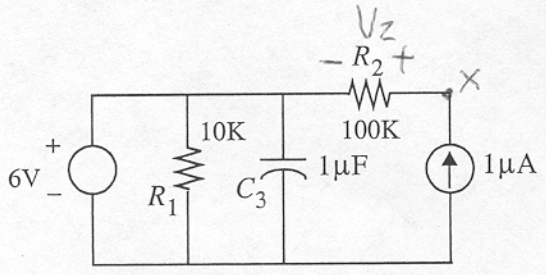(d) P_4 , the power into the current source.

$P_4 = -6.1 \mu\text{W}$

- ① First, Find V_2 , voltage drop across R_2 .
- ② Second, find V_x
- ③ third, use $P = IV$



① $V_2 = IR = (1 \mu\text{A})(100K) = 0.1V$



② $V_x = 6V + V_2 = 6V + 0.1V = 6.1V$

③ $P = IV = -(1 \mu\text{A})(6.1V) = -6.1 \mu\text{W}$

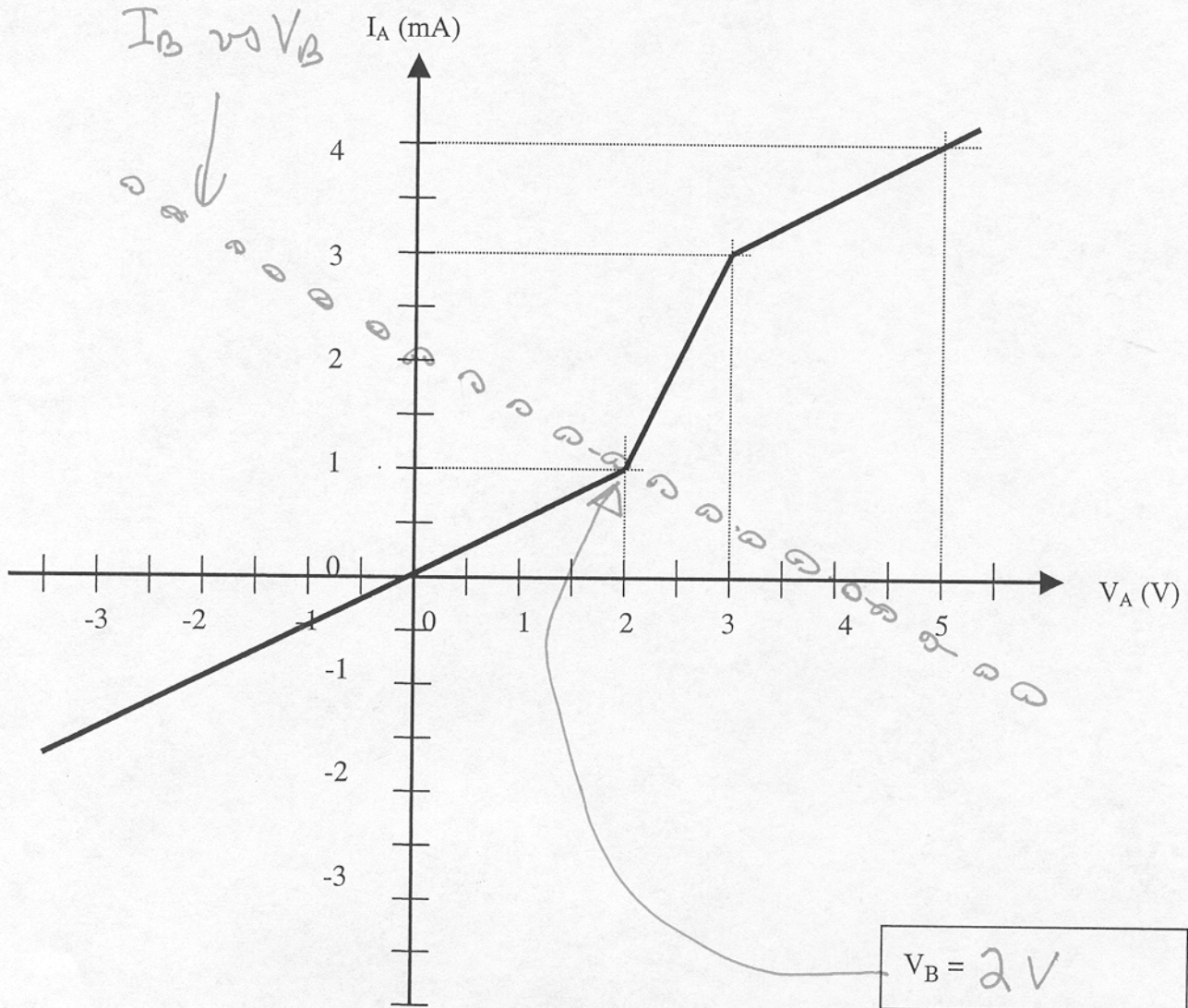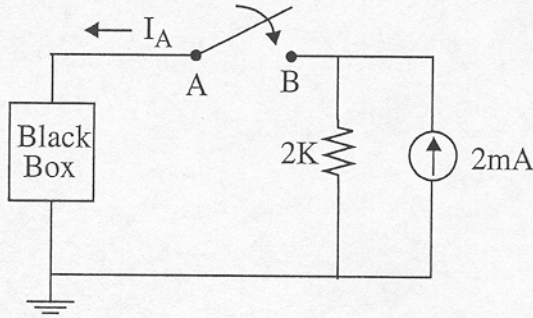Problem 5 (20 points)


The circuit below consists of two parts: 1) a “black box” that has the nonlinear I-V characteristics shown on graph I_A versus V_A , and 2) a simple resistor in parallel with a current source. When the switch is open, it is obvious that $V_A = 0$ and $V_B = 4V$.

Use the load-line method to find the approximate value of V_B when the switch is closed. (IMPORTANT: You must show your work to receive credit.) (Also note: This is a DC problem, not a transient problem.)




Problem 5 Worksheet

Solution:

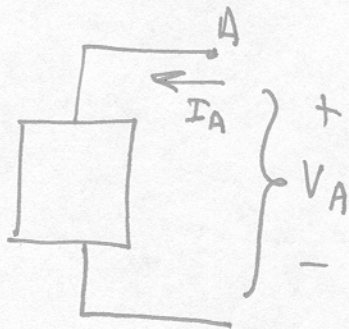

I_A vs V_A shown on graph

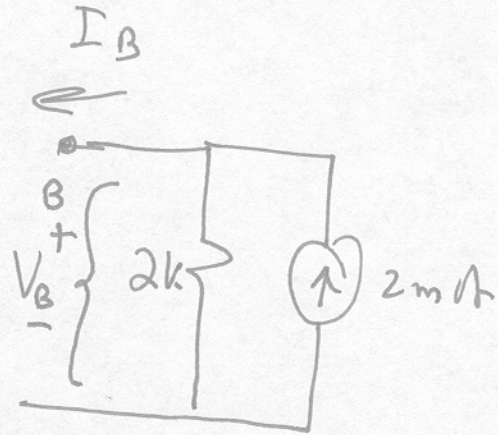

I_B vs V_B is linear
and $I_B = 2\text{mA}$ when $V_B = 0$
and $I_B = 0$ when $V_B = 4\text{V}$
WE PLOT THIS ON
SAME AXES ○○○○○

BUT $I_B = I_A$

& $V_B = V_A$

SO

INTERSECTION IS SOLUTION